

# $A_4$

## Assignment IV

Prof. Dr. P. Tang; Computer Organization I

Connor Taffe

November 12, 2015

1. The block diagram is sketched and attached to this assignment. The function table in figure 1 shows the output of the ALU in relation to the inputs  $x$ ,  $y$ , and  $z$  and the controls  $S_{0-2}$ . Note the  $x$  in the controls column is a placeholder for any value, and not the input  $x$ .

| $S_0$ | $S_1$ | $S_2$ | ALU          |
|-------|-------|-------|--------------|
| 0     | 0     | 0     | $x + y$      |
| 0     | 0     | 1     | $x - y$      |
| 0     | 1     | 0     | $x \wedge y$ |
| 0     | 1     | 1     | $x$          |
| 1     | 0     | $x$   | $y$          |
| 1     | 1     | $x$   | $z'$         |

Figure 1: Truth table for ALU

2. Figure 2 shows the internal circuitry of the ALU. Notice that I have made a design decision alternate to that made in lecture five by bundling the negation of  $z$  into the ALU. I understand that in a real situation, the Control Unit would have to coordinate the operations of more than one operational unit e.g. an FPU. For this reason, I will use an external not to create  $z'$ , to give the Control Unit something else to control.
3. The datapath diagram is sketched and attached to this assignment. The control points are  $S_{0-2}$  for controlling the operation of the ALU, and loads for  $x$ ,  $y$ , and  $z$ .
4. Figure 3 shows the internal circuitry of the datapath.
5. Figure 4 is the control point table which includes all six operations and their relevant control points settings.
6. Figure 6 shows the internal circuitry of the Control Unit.

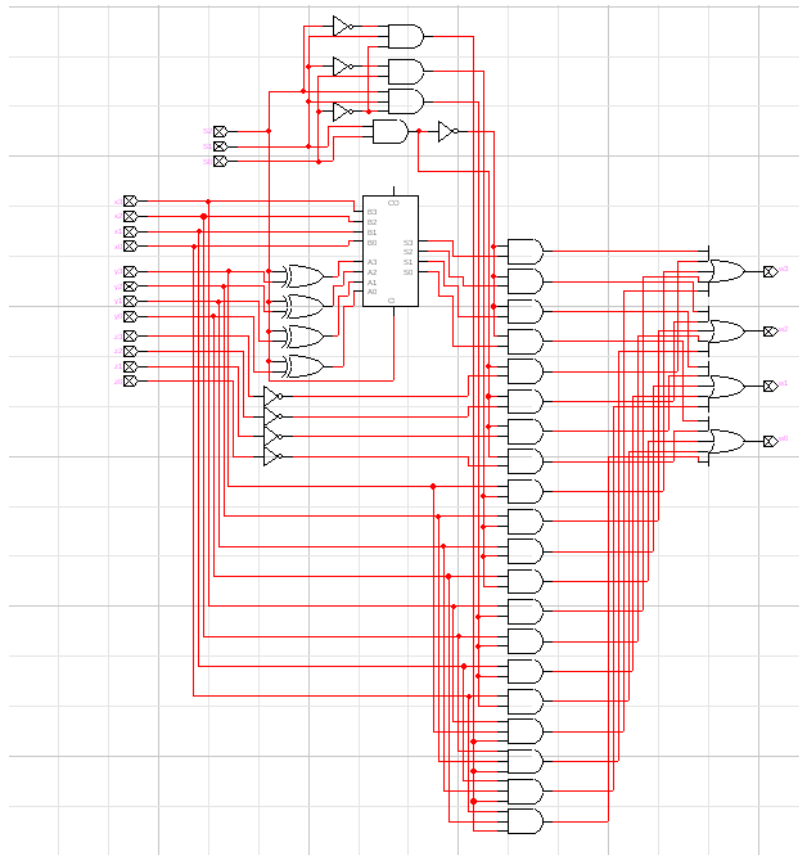


Figure 2: Internal circuit of the ALU

7. (a) I set the registers to the appropriate numbers. The testing circuit in the next question is photographed with those properties.
- (b) Figure 7 shows the testing circuit.
- (c) The calculations are shown in figure 8.
- (d) Figure 9 waveform shows the testing. As you can see, the registers simulate with a fuzzy value after a few iterations. I have used those same registers before and they performed well. The circuit seems valid and the CU is making correct decisions. I also tested the ALU several times and it also seems to function properly. I have no idea what is causing the blurring. I have retried the simulation several times. Also the  $g$  signal for  $x$  is not shown properly as it is possibly labeled incorrectly. But you can see from the values propogating to it that it is functioning properly.

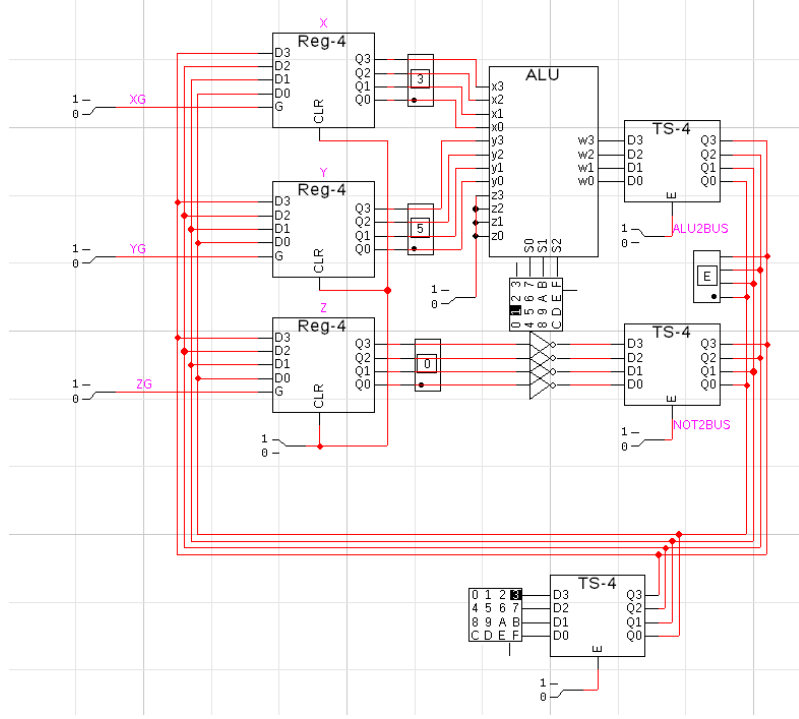


Figure 3: Internal circuit of the datapath

|            |                           | $S_0$ | $S_1$ | $S_2$ | load $x$ | load $y$ | load $z$ | ALU to bus | not to bus |
|------------|---------------------------|-------|-------|-------|----------|----------|----------|------------|------------|
| $\alpha$   | $x \leftarrow x + y$      | 0     | 0     | 0     | 1        | 0        | 0        | 1          | 0          |
| $\beta$    | $y \leftarrow x - y$      | 0     | 0     | 1     | 0        | 1        | 0        | 1          | 0          |
| $\gamma$   | $x \leftarrow x \wedge y$ | 0     | 1     | 0     | 1        | 0        | 0        | 1          | 0          |
| $\delta$   | $z \leftarrow x$          | 0     | 1     | 1     | 0        | 0        | 1        | 1          | 0          |
| $\epsilon$ | $x \leftarrow y$          | 1     | 0     | 0     | 1        | 0        | 0        | 1          | 0          |
| $\theta$   | $x \leftarrow z'$         | 1     | 1     | 0     | 1        | 0        | 0        | 0          | 1          |

Figure 4: Control Point table

$$\begin{aligned}
S_0 &= \epsilon + \theta & (1) \\
S_1 &= \gamma + \delta + \theta & (2) \\
S_2 &= \beta + \delta & (3) \\
\text{load } x &= \alpha + \gamma + \epsilon + \theta & (4) \\
\text{load } y &= \beta & (5) \\
\text{load } z &= \delta & (6) \\
\text{ALU to bus} &= \alpha + \beta + \gamma + \delta + \epsilon & (7) \\
\text{not to bus} &= \theta & (8)
\end{aligned}$$

(9)

Figure 5: Boolean equations for controls

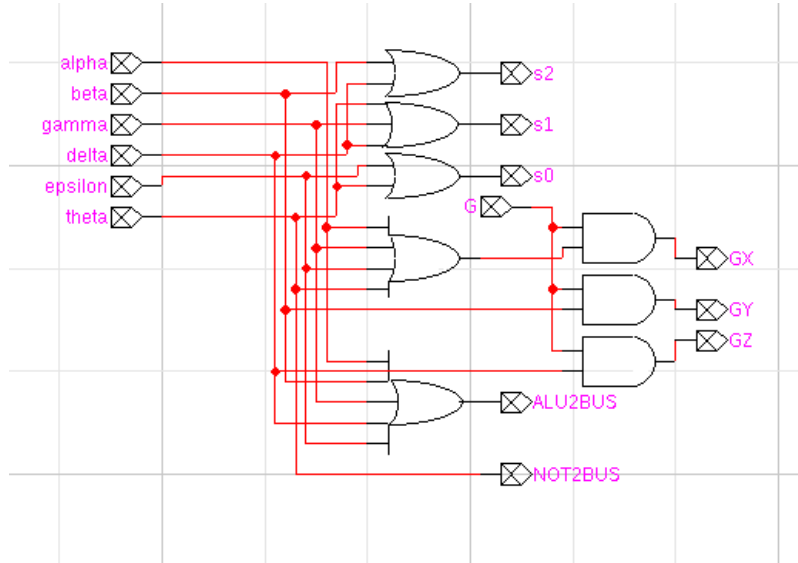


Figure 6: Internal circuit of the control unit



$$(19)$$

5

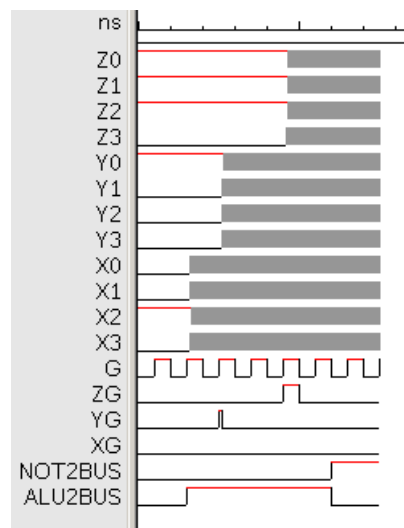


Figure 9: Waveform for circuit