

# $L_4$

## Laboratory IV

Prof. Dr. P. Tang, CS 3482: Comp. Org. I

Connor Taffe, T no. 3742

April 21<sup>st</sup>, 2015

### 1 Details of Lab 4

**Q. 1 C.** Change the gate-delay of the AND gate to 0, 3, 5. Observe the output changes with respect to the changes of input  $x$ .

They mimic the input  $x$  with an offset along the time axis associated with the time of the gate delay.

**Q. 2** Here follows the Karnaugh map of  $f$ .

$$f(a, b, c, d) = (a' + b)'c + d(b' + ac)$$

		$CD$			
		00	01	11	10
$AB$	00	0	1	1	0
	01	0	0	0	0
	11	0	0	1	0
	10	0	1	1	1

Which shows that  $f$  can be represented as the sum of minterms as follows:

$$f(a, b, c, d) = b'd + acd + ab'c$$

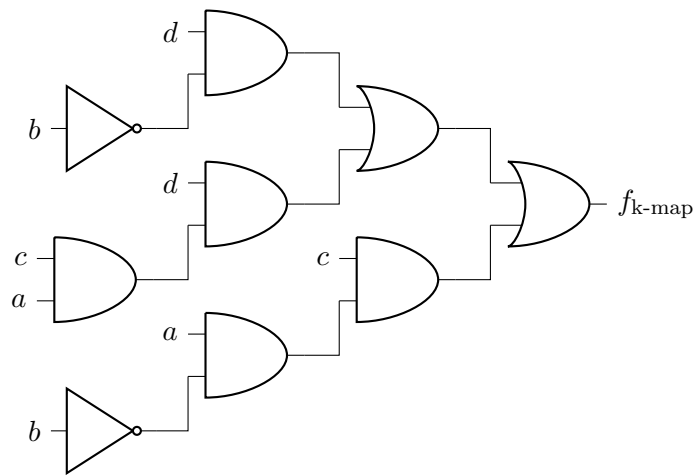


Figure 1: Circuit diagram for  $f$  after reduction to sum of midterms.