

# $L_4$

## Laboratory IV

Prof. Dr. P. Tang, CS 3482: Comp. Org. I

Connor Taffe, T no. 3742

April 21<sup>st</sup>, 2015

## 1 Details of Lab 4

**Q. 1 C.** Change the gate-delay of the AND gate to 0, 3, 5. Observe the output changes with respect to the changes of input  $x$ .

The output mimics the input  $x$  with an offset along the time axis associated with the time of the gate delay. E.g. a 3ns gate delay results in a 3ns shift between the input  $x$  and the output.

**Q. 2** Draw the circuit to implement the Boolean function as follows

$$f(a, b, c, d) = (a' + b)'c + d(b' + ac)$$

according to the expression directly. Connect  $b$ ,  $c$  and  $d$  to binary switches and make them to be 0, 1 and 0, respectively. Connect  $a$  to a clock.

**Q. 2.1** According to your simulation, how much time does it take for the change of  $a$  to be reflected in the output  $f$ ?

Five nanoseconds.

**Q. 2.2** Change the gate delays of all the gates along the path from  $a$  to  $f$  to 0, 2 and 4. Verify that the total delays from  $a$  to  $f$  you observed are correct.

For a 0ns delay,  $a$  and  $f$  corresponded exactly. For a 2ns delay,  $a$  and  $f$  differed by a 10ns delay. For a 5ns delay,  $a$  and  $f$  differed by a 45ns delay.

**Q. 3** Here follows the logical truth table (figure 1), Karnaugh map (figure 2), and direct circuit implementation (figure 3) of said K. map of  $f$ .

$$f(a, b, c, d) = (a' + b)'c + d(b' + ac)$$

Which shows that  $f$  can be represented as the sum of minterms as follows:

$$f(a, b, c, d) = b'd + acd + ab'c$$

**Q. 4** Compare the circuits.

Testing all 16 possible input combinations resulted in identical outputs if the gate delay is set to 0ns.

$a$	$b$	$c$	$d$	$a' + b$	$(a' + b)'c$	$ac$	$b' + ac$	$d(b' + ac)$	$(a' + b)'c + d(b' + ac)$
1	1	1	1	1	0	1	1	1	1
1	1	1	0	1	0	1	1	0	0
1	1	0	1	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0
1	0	1	1	0	1	1	1	1	1
1	0	1	0	0	1	1	1	0	1
1	0	0	1	0	0	0	1	1	1
1	0	0	0	0	0	0	1	0	0
0	1	1	1	1	0	0	0	0	0
0	1	1	0	1	0	0	0	0	0
0	1	0	1	1	0	0	0	0	0
0	1	0	0	1	0	0	0	0	0
0	0	1	1	1	0	0	1	1	1
0	0	1	0	1	0	0	1	0	0
0	0	0	1	1	0	0	1	1	1
0	0	0	0	1	0	0	1	0	0

Figure 1: Truth table for  $(a' + b)'c + d(b' + ac)$

		$CD$			
		00	01	11	10
$AB$	00	0	1	1	0
	01	0	0	0	0
	11	0	0	1	0
	10	0	1	1	1

Figure 2: Karnaugh map of figure 1

 


Figure 3: Circuit diagram for  $f$  after reduction to sum of midterms.