

A_2
Assignment 2

CS 3482; Professor Tang

Connor Taffe. T no. 3742

November 3, 2015

1. To test the circuits, we will assure that the Q only changes when G is 1 and D is changed. Q should reflect the value of D while G is on, and then lock when Q is 0. G should serve as the *latch* in the D latch circuit.

The D flip flop is edge triggered rather than level triggered as the D latch is. This means that the D flip flop should only change on rising edges of G . Q only reflects D if it is at the rising edge of G , otherwise it is locked.

- 2.
3. Each row of output D bits is the input Q bits of the last state plus 1. The sum of minterms obtained from the Karnaugh maps of each of the four D s are as follows:

$$D_0 = Q'_0$$

$$D_1 = Q'_0Q_1 + Q_1Q'_1$$

$$D_2 = Q'_3Q'_2Q_1Q_0 + Q'_3Q_2Q'_1 + Q'_3Q_2Q_1Q'_0 + Q_3Q_2Q_1Q_0 + Q_3Q'_2Q'_1 + Q_3Q'_2Q_1Q'_0$$

$$D_3 = Q_3Q_2 + Q_3Q'_2Q'_1 + Q_3Q'_2Q_1Q'_0 + Q'_3Q_2Q_1Q_0$$