

$A_1$   
Assignment 1

CS 3482; Professor Tang

Connor Taffe. T no. 3742

April 21<sup>st</sup>, 2015

## 1 Question

Draw the circuit in LogicWorks to implement the Boolean function:

$$f(a, b, c, d) = (a' + b)'c + d(b' + ac)$$

Figure 1: Given boolean function  $f$

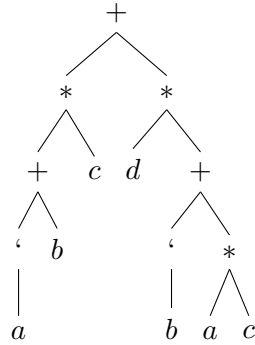


Figure 2: Parse tree of figure 1

 
 




Figure 3: LogicWorks implementation of  $f$

- (a) Figure 2 shows the structure of a naive circuit implementation. Figure 3 shows the LogicWorks implementation of the circuit.
- (b) I observed an 18ns delay between  $a$  and  $f$  (shown in figure 4). This is because the gate delays between  $a$  and  $f$  accumulate.

Figure 4: LogicWorks implementation of  $f$ , waveforms

## 2 Question

Simplify the same Boolean function in figure 1 to be the sum of its minterms by obtaining its truth table first.

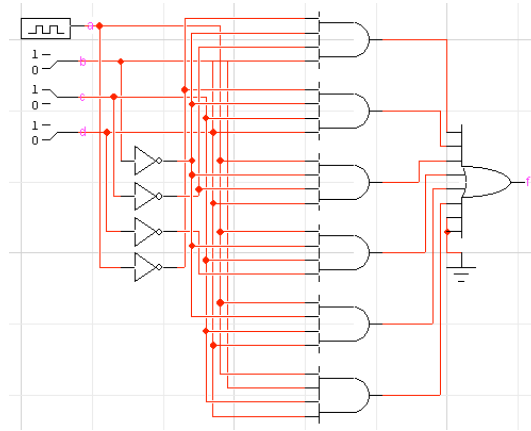 
Figure 5: LogicWorks implementation of  $f_{\text{minterm}}$ Figure 6: LogicWorks implementation of  $f_{\text{minterm}}$ , waveforms

- Figure 1 shows the truth table for the function.
- $f_{\text{minterm}} = a'b'c'd + a'b'cd + ab'c'd + ab'cd' + ab'cd + abcd$
- Figure 7 shows the parse tree and thusly the gate implementation of the minterms of  $f$ . The LogicWorks circuit is represented in figure 5.
- I observed a delay of 4ns between  $a$  and  $f$  (shown in figure 6). This is because the delays between  $a$  and  $f$  accumulate as in the naive implementation, but less so as there is a maximum of three gates in the path between  $a$  and  $f$ .

## 3 Question

- Figure 8 shows the trees of a 2-to-4 decoder with an active-high enable  $E$ . Testing is shown in figure 10, and the tested circuit LogicWorks implementation is shown in figure 9.

$a$	$b$	$c$	$d$	$a'$	$a' + b$	$(a' + b)'$	$(a' + b)'c$	$ac$	$b'$	$b' + ac$	$d(b' + ac)$	$f$
0	0	0	0	1	1	0	0	0	1	1	0	0
0	0	0	1	1	1	0	0	0	1	1	1	1
0	0	1	0	1	1	0	0	0	1	1	0	0
0	0	1	1	1	1	0	0	0	1	1	1	1
0	1	0	0	1	1	0	0	0	0	0	0	0
0	1	0	1	1	1	0	0	0	0	0	0	0
0	1	1	0	1	1	0	0	0	0	0	0	0
0	1	1	1	1	1	0	0	0	0	0	0	0
1	0	0	0	0	0	1	0	0	1	1	0	0
1	0	0	1	0	0	1	0	0	1	1	1	1
1	0	1	0	0	0	1	1	1	1	1	0	1
1	0	1	1	0	0	1	1	1	1	1	1	1
1	1	0	0	0	1	0	0	0	0	0	0	0
1	1	0	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	1	0	1	0	0
1	1	1	1	0	1	0	0	1	0	1	1	1

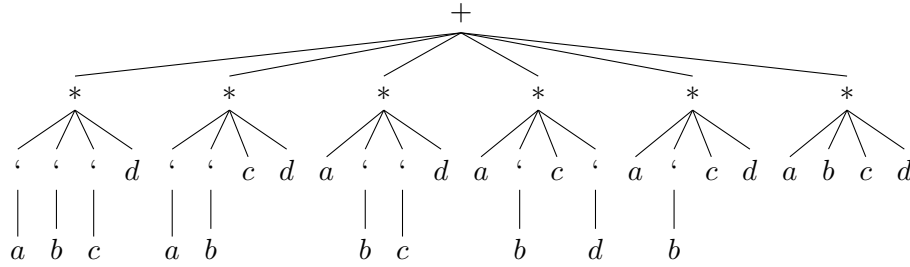Table 1: Truth table for  $f$  as described in figure 1Figure 7: Parse tree of minterms of  $f$ 

- (b) Testing is shown in figure 12, and the tested circuit LogicWorks packaged implementation is shown in figure 11.

## 4 Question

- (a) Five, one for the first two bits, and four for each of the four minterms of the first two bits.
- (b) Figure 15 shows the parse trees of a 4-to-16 decoder built only using 2-to-4 decoders. The parse tree describes the gate diagram. The LogicWorks implementation can be seen in figure 13.
- (c) Figure 14 shows the waveform.

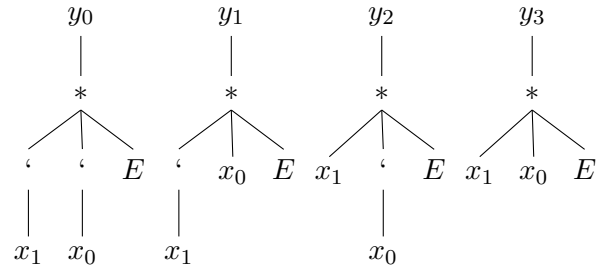


Figure 8: Parse trees of 2-to-4 decoder with an active-high enable  $E$

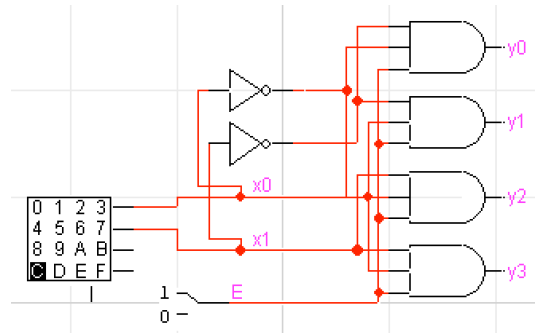


Figure 9: Internal circuit of a 2-4 decoder; being tested.

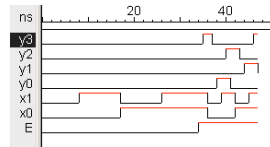


Figure 10: Test waveform output of a 2-4 decoder.

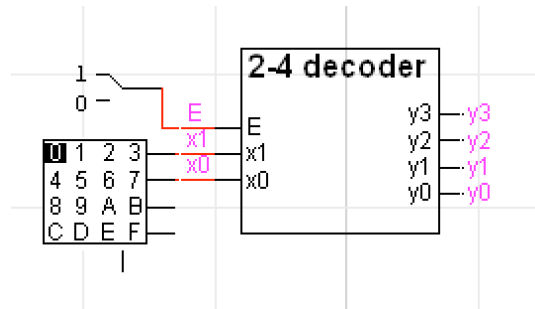


Figure 11: Internal circuit of a 2-4 decoder (packaged); being tested.

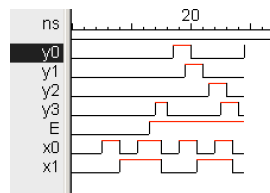


Figure 12: Test waveform output of a 2-4 decoder (packaged).

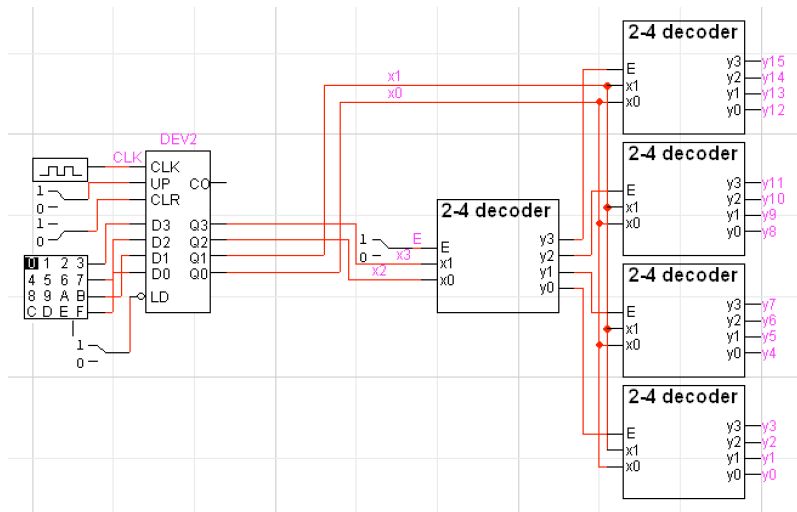


Figure 13: Internal circuit of a 4-16 decoder; being tested.

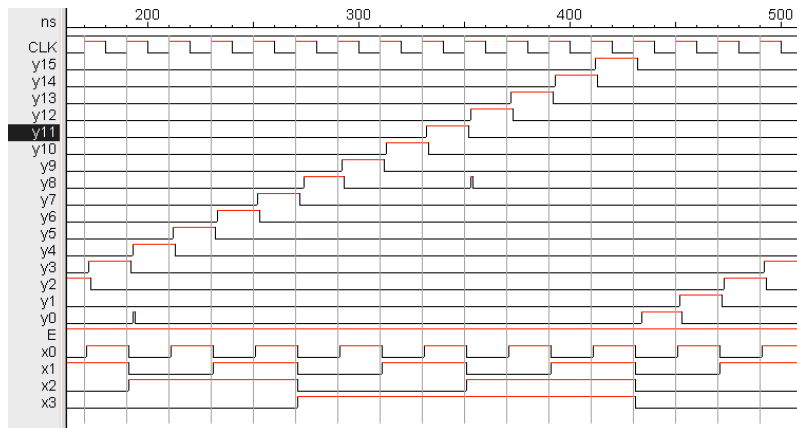


Figure 14: Test waveform output of a 4-16 decoder.

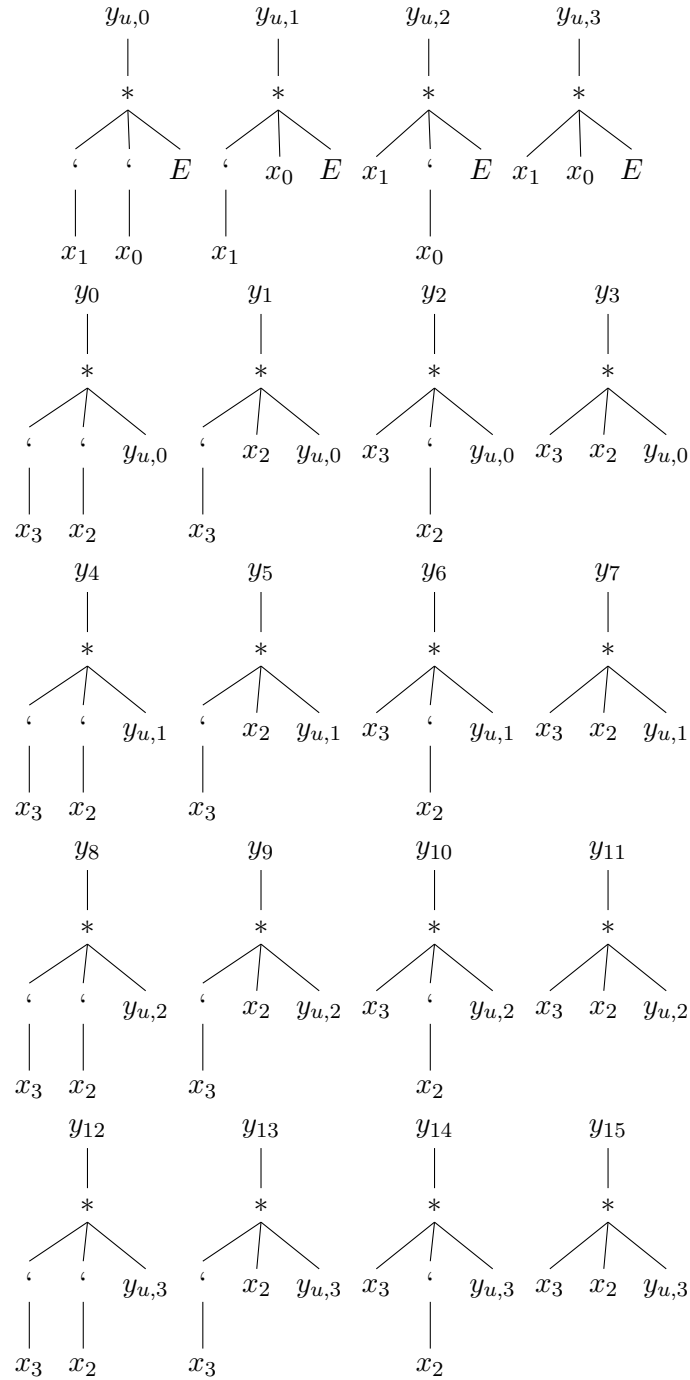


Figure 15: Parse trees of 4-to-16 decoder with an active-high enable  $E$ . For convenience and space the first line depicts the inner 2-to-4 decoder for the first two bits, denoted with subscript  $u$ .